

---

# **DESIGN AND ANALYSIS OF CMOS LOGIC GATES IN CADENCE VIRTUOSO TOOL**

- **Presented By: Vinayak Agrawal**
- **Roll No.: 21BIT044**
- **Presented To: AMIT M KUMAR**

# INTRODUCTION

## Overview of CMOS Technology:

- CMOS (Complementary Metal-Oxide-Semiconductor) combines NMOS and PMOS transistors to create efficient digital logic circuits.
- Widely used in VLSI design due to its low power consumption and high noise immunity.

## Objectives of the Presentation:

- Focuses on the design and transient analysis of basic logic gates (Inverter, OR, NOR, AND, NAND) using CMOS technology.
- Showcasing the use of Cadence Virtuoso for CMOS circuit design and simulation.


# LITERATURE WORK

- **CMOS Fundamentals:**






- CMOS technology is preferred due to its low power consumption and high noise immunity.
- NMOS transistors are used to pull the output down (0), while PMOS transistors are used to pull the output up (1).

 - **Recent Trends in CMOS VLSI:**

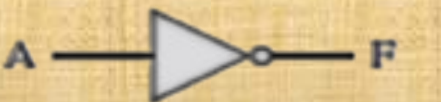- **Scaling challenges:** As transistors shrink, problems like short-channel effects and leakage currents increase.
- **Advancements:** Innovations like FinFET, SOI (Silicon-On-Insulator) have helped overcome some scaling limitations.





Name	Graphical Symbol	Algebraic Function	Truth Table															
AND		$F = A \cdot B$ or $F = AB$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = A + B$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$F = \overline{A}$ or $F = A'$	<table><tr><th>A</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
NAND		$F = \overline{AB}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
A	B	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = \overline{A + B}$	<table><tr><th>A</th><th>B</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	F	0	0	1	0	1	0	1	0	0	1	1	0
A	B	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

# METHODOLOGY

- **Designing CMOS Logic Gates in Cadence Virtuoso:**

Step-by-step design of Inverter, OR, NOR, AND, NAND gates using NMOS and PMOS transistors.

- **Simulation and Transient Analysis:**

Transient analysis is performed to observe the switching behavior of the gates, showing how the output transitions over time with varying inputs.



- **Tools used:**

Cadence Virtuoso for schematic capture and simulation.

The Cadence logo is displayed in a white rounded rectangle. It features the word "cadence" in a lowercase, sans-serif font. A red horizontal bar is positioned above the letter "a", and a small registered trademark symbol (®) is located to the upper right of the letter "e".
  
# DESIGN & RESULTS


BASIC LOGIC GATES (INVERTER, OR, NOR, AND, NAND)






# INVERTER

## 1 PMOS & 1 NMOS connected in series

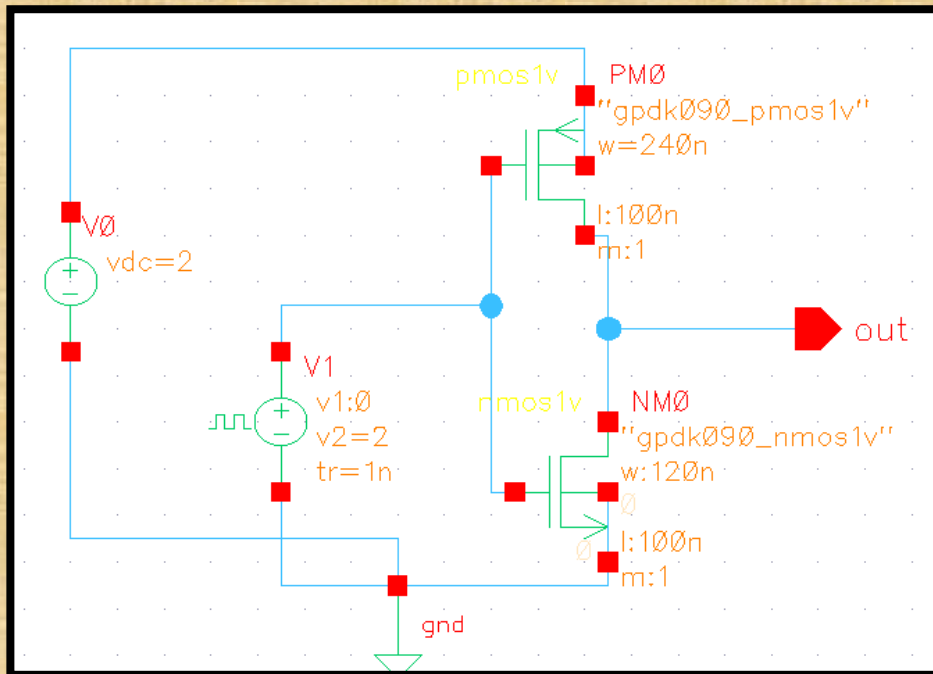


 
- Graph showing the input switching between 0 and 1, with corresponding output switching inversely.
- Inverter shows perfect switching behavior with minimal delay.


 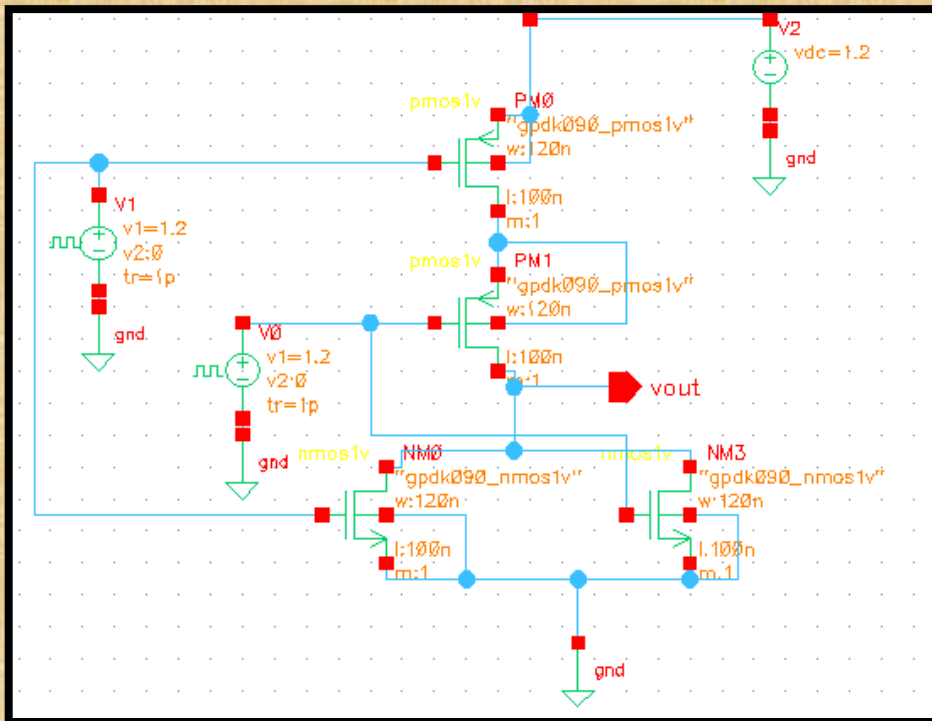
# NOR GATE

2 PMOS in series & 2 NMOS in parallel  
connected together in series


- NOR gate outputs low when either input is high.





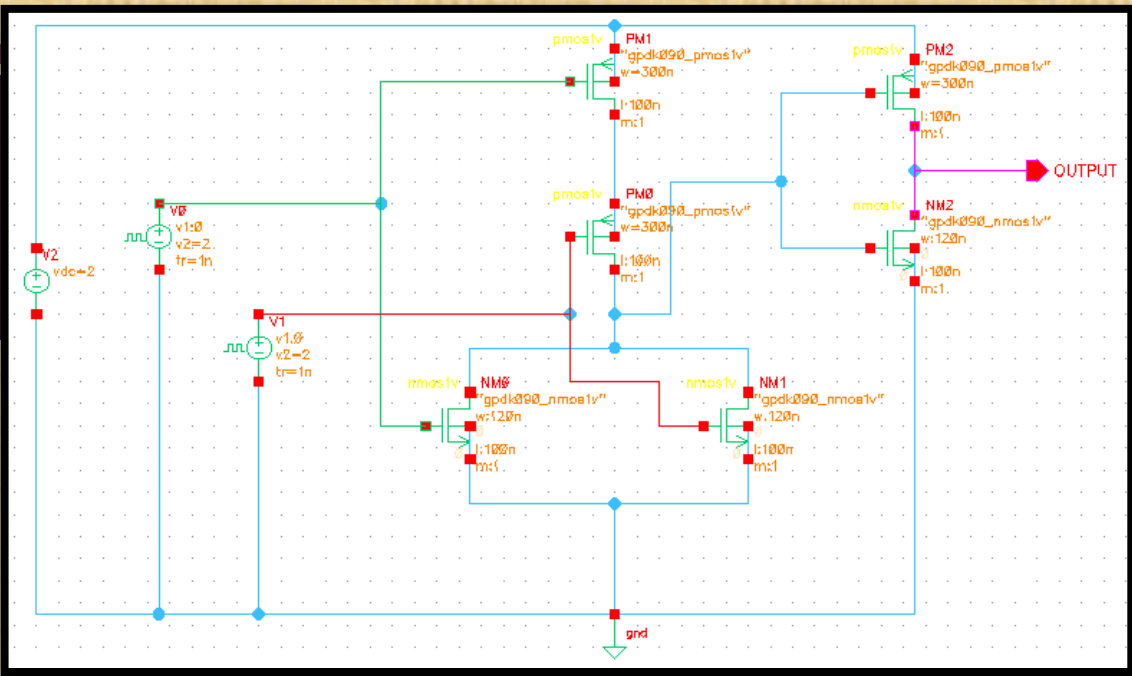
# OR GATE

2 PMOS in series & 2 NMOS in parallel connected together in series & inverter connected before output.




 
- OR gate output follows the logical OR behavior, outputting 1 when any input is 1.


 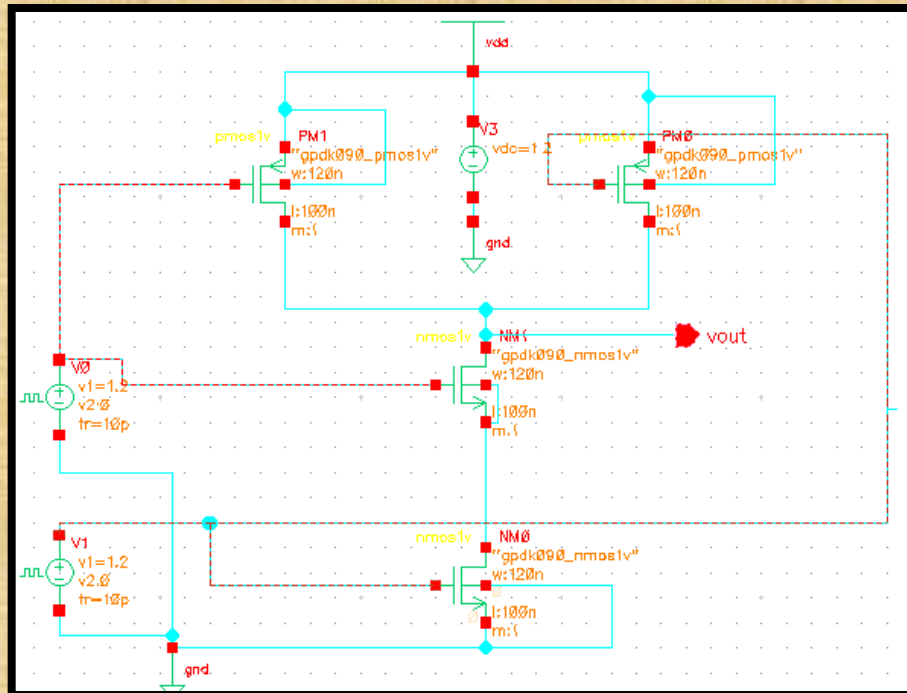
# NAND GATE


2 PMOS in parallel & 2 NMOS in series connected together in series.

- NAND gate output is high except when both inputs are high.



 
# AND GATE

2 PMOS in parallel & 2 NMOS in series connected together in series & inverter connected before output



 - AND gate outputs high only when both inputs are high.





# CONCLUSION

## ■ Key Points:

- Successfully designed and simulated basic CMOS logic gates (Inverter, OR, NOR, AND, NAND) in Cadence Virtuoso.
- The transient analysis graphs confirm the correct logical behavior of each gate.

## ■ Why CMOS is Efficient:

- CMOS consumes power only during switching, making it more power-efficient compared to other technologies.

## ■ Future Prospects:

- As technology scales down, challenges such as leakage current need to be addressed.
- CMOS will continue to evolve with new designs like FinFETs for more power-efficient and faster circuits.

## REFERENCES

- **CMOS VLSI Design: A Circuits and Systems Perspective** – Neil H. E. Weste and David Harris.
- **Digital Integrated Circuits: A Design Perspective** – Jan M. Rabaey.
- **Cadence Virtuoso Documentation** for design and simulation methodology.
- CMOS VLSI Design faculty guidance.

THANK YOU!!!

